


1)

f [Hz]	50	100	200
r [Ω]	100 k	100 k	100 k
I [A]	99,9 μ	100,4 μ	98,08 μ
$V_{PP} = 2V_L$	87,2 m	170 m	340 m
V_R	20,8 m	26 m	52 m
L	4,36	4,24	4,33
R	208,2	259,84	530,12
V	10,1	10,2	10,2

$$L = \frac{V_{PP}}{4 \cdot I \cdot f}$$

$$I = \frac{V - (V_R + V_{PP})}{r}$$


$$R = \frac{V_R}{I}$$

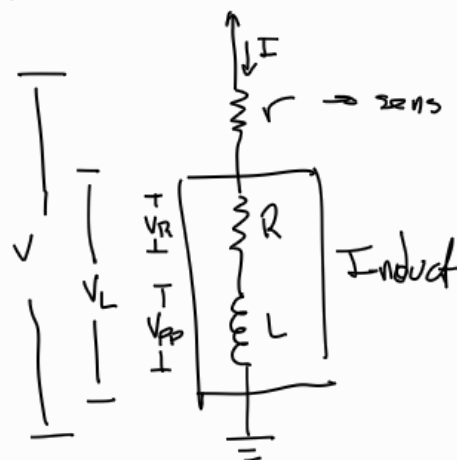

NewFile	f
0	50
1	100
2	200

2)

f [Hz]	10 k	10 k	10 k
C [F]	1 μ	2,2 μ	4,7 μ
r [Ω]	1 k	1 k	1 k
V_C	300 m	180 m	98,4 m
$I = \frac{V}{r}$	10,2 m	10,2 m	10,2 m
V_R	30 m	38 m	24,8 m
$RSE = \frac{V_R}{I}$	2,94	3,72	2,43
V	10,2	10,2	10,2

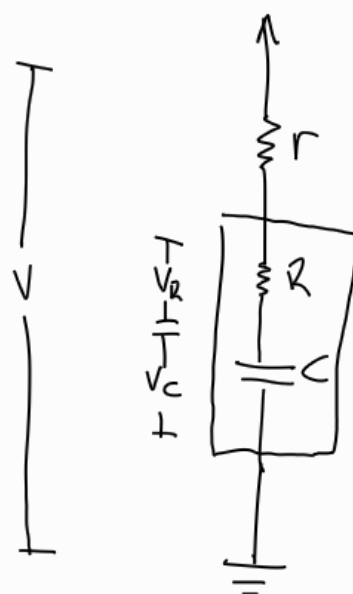

$$V_R = I \cdot RSE$$

NewFile	f
3	1 μ
4	2,2 μ
5	4,7 μ

3) condic.

	f	C_c	C_T	$Q = C_c / C_T$
$f_1 (\sqrt{2} \cdot C_{MAX})$	18 k	464 m	2,56	0,1812
$f_0 (C_{MAX})$	11,8 k	600 m	3,64	0,1813
$f_2 (\sqrt{2} \cdot C_{MAX})$	2	456 m	4,64	0,0982

NewFile	f
6	f_2
7	f_0
8	f_1

